

*Total number of printed pages-3*

**1 SEM BCA (CBCS) DD 1-3**

**2024**

**( December )**

**COMPUTER APPLICATION**

**Paper : 1-3**

**( Digital Design )**

**Full Marks : 60**

**Time : Three hours**

***The figures in the margin indicate  
full marks for the questions.***

1. Answer the following : 1×5=5
- (a) Define logic gate.
  - (b) Write the characteristics equation of JK Flip-Flop.
  - (c) What is binary number ?
  - (d) Define Hamming distance.
  - (e) Convert  $(237)_8$  to decimal.

*Contd.*

2. (a) Construct a full subtractor circuit and simplify the equation using K-map.

7

**Or**

Construct an 8-to-1 multiplexer. Explain briefly.

- (b) Explain about weighted codes with examples.

5

- (c) Convert the following :

$1 \times 3 = 3$

(i)  $(167)_{10}$  to binary

(ii)  $(1723)_8$  to binary

(iii)  $(649)_{16}$  to binary

3. Answer **any four** questions from the following :

$5 \times 4 = 20$

(a) Explain about error detection method.

(b) Explain 1-to-4 demultiplexer with logic diagram and truth table.

(c) Explain 3-to-8 line decoder with logic diagram and truth table.

- (d) Explain about Octal to Binary Encoder with logic diagram and truth table.

- (e) Write the steps for designing a combinational circuit.

4. (a) Define Flip-Flop. Draw and explain about JK Flip-Flop.

$1+5=6$

**Or**

Define latch. Explain about S-R latch with logic diagram and truth table.

$1+5=6$

- (b) Explain about asynchronous down counter.

6

- (c) Simplify the expression —  
 $Y = \sum m(8,10,11,12,13,14,15)$  using K-map.

4

- (d) Explain about Shift Register.

4

**Or**

Explain about DeMorgan's theorem.